

Your name Ambika Murali

83

CS 350 Midterm Exam, Mon Mar 7, 2011

(75 minutes, 100 points total)

Instructions

This exam is closed book, one 8.5"×11" page of notes (both sides). No sharing notes and no equipment (calculators, phones, music players, etc). The usual penalty for copying or sharing answers on a quiz or exam is a final grade of E for the course. If you have any questions, please ask during the quiz, not after.

Short Answer Questions [points as marked]

1. [8 pts] For each of the three schemes for representing negative numbers, (a) What decimal value does 1000 0000 represent? (b) Is 1000 0000 the most negative number in this scheme?

a.) signed: -64

1's: -127

2's: 10000000

60111111

10000000

b.) 10000000 is the most negative in the 1's complement, and 2's complement

2. [8 pts] Let octal 111 represent a 7-bit 2's complement number. (a) What is the decimal value of this number? (b) Translate this number into 8-bit 2's complement hexadecimal. What is the result?

111

01001001

a.) 1001001
60110110
+ 1

0110111
6 5 4 3 2 1 0

$(1 \times 2^0) + (1 \times 2^1) + (1 \times 2^2) + (0 \times 2^3) + (1 \times 2^4) + (1 \times 2^5) + (0 \times 2^6)$
 $= 1 + 2 + 4 + 16 + 32$
 $= 55$

sign extend
 1001001_2
to $11001001_2 = C9_{16}$

b.) 11010111

600101000

1

00101001

2 9

hex: 29

-55 mi + 55

- B9 B-1011
9-1001

minuscule ↓

$$\begin{array}{r} 10111001 \\ 6) 01000110 \\ + \end{array}$$

$$(1 \times 2^0) + (1 \times 2^1) + (1 \times 2^2) + (0 \times 2^3) + (0 \times 2^4) + (0 \times 2^5) + (1 \times 2^6) + (0 \times 2^7)$$

and the scientific notation

$$5 \frac{1}{4} = 0.25$$

- $$V_2 = 0.5 \quad \frac{1}{4} = 0.25$$

$$S = 1 + 2 + 4 + \dots + 64 = 127$$

$$\begin{array}{r} 2 \overline{) 25} \quad 1 \\ 2 \overline{) 12} \quad 6 \\ 2 \overline{) 6} \quad 3 \\ 2 \overline{) 3} \quad 1 \\ 2 \overline{) 2} \quad 1 \\ 2 \overline{) 1} \quad 0 \end{array}$$

inconsistent
you're
reading
downward
should be
upward
1 not 10011

$1101001 \cdot (0 \times 2^{-1}) - (1 \times 2^{-2}) - (1 \times 2^{-3})$
 0.55
 1.101001091×2^4 *consistent*
 20

- 110.001
1.10001 $\times 2^2$

bit 1

exponent: $10 + 127$

$= 137$ 1000 1001
b m: ~~X~~ 1000 1001


2 $\overline{)137}$ 1
2 $\overline{)68}$ 0
2 $\overline{)34}$ 0
2 $\overline{)17}$ 1
2 $\overline{)8}$ 0
2 $\overline{)4}$ 0
2 $\overline{)2}$ 0
2 $\overline{)1}$ 1

Fraction: $101\ 000000000000\ \frac{0}{10}\ \frac{0}{10}\ \frac{0}{10}\ \frac{0}{10}\ \frac{0}{10}$

~~1~~ 1000100110100000000000000000000000 ✓

6. [6 pts] Draw a PLA-based logic gate implementation for output X from inputs A , B , and C as specified by the table to the right.

A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

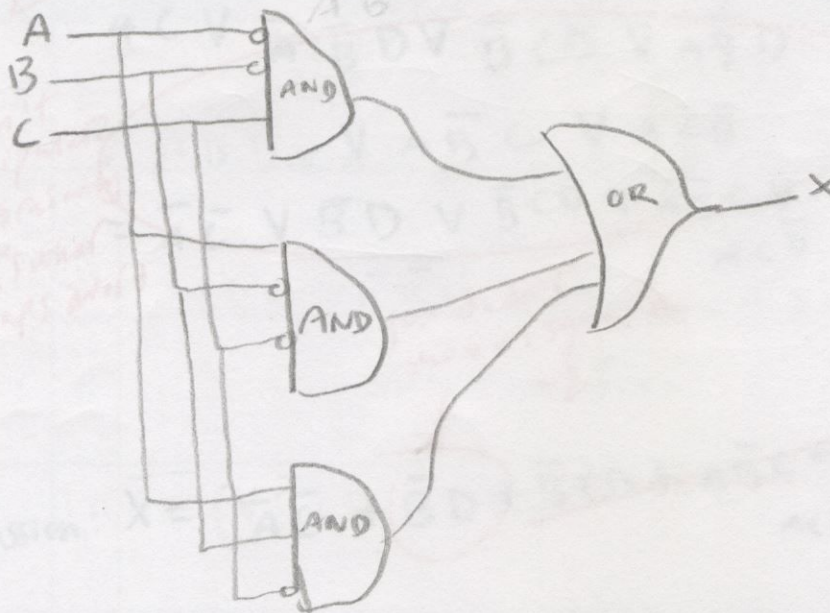

7. [14 pts] Take the truth table to the right, draw a Karnaugh map for output X from inputs A , B , C , and D , select implicants, and translate your implicants to a simplest boolean expression for X .

A	B	C	D	X
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

Handwritten Karnaugh map for output X :

	CD	00	01	11	10
AB	00	1	1	1	0
	01	1	1	0	0
	11	0	0	0	1
	10	0	1	1	1

Implicants

$\bar{B}D$ square -2

$\bar{A}\bar{C}$ V $\bar{A}\bar{B}D$ V $\bar{B}CD$ V $A\bar{B}D$


redundant -1

Don't manipulate algebraically. That's what K maps avoid

you didn't show as square -2


Expression: $X = (\bar{A}\bar{C} + \bar{B}D + \bar{B}CD + A\bar{B}C + A\bar{C}D)$

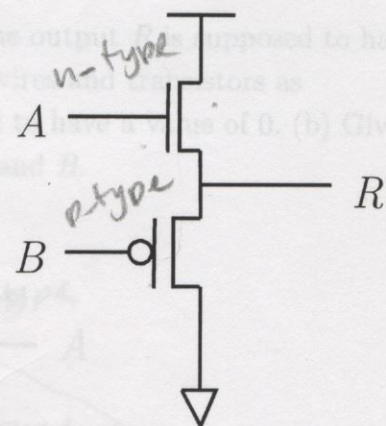8. [8 pts] Inspect the transistor diagram to the right. Fill in the table below: For each combination of A and B , specify whether the result R is a logical 0, a logical 1, or if we have a short circuit or an open circuit.



A	B	R
0	0	0
0	1	open circuit
1	0	short circuit
1	1	1

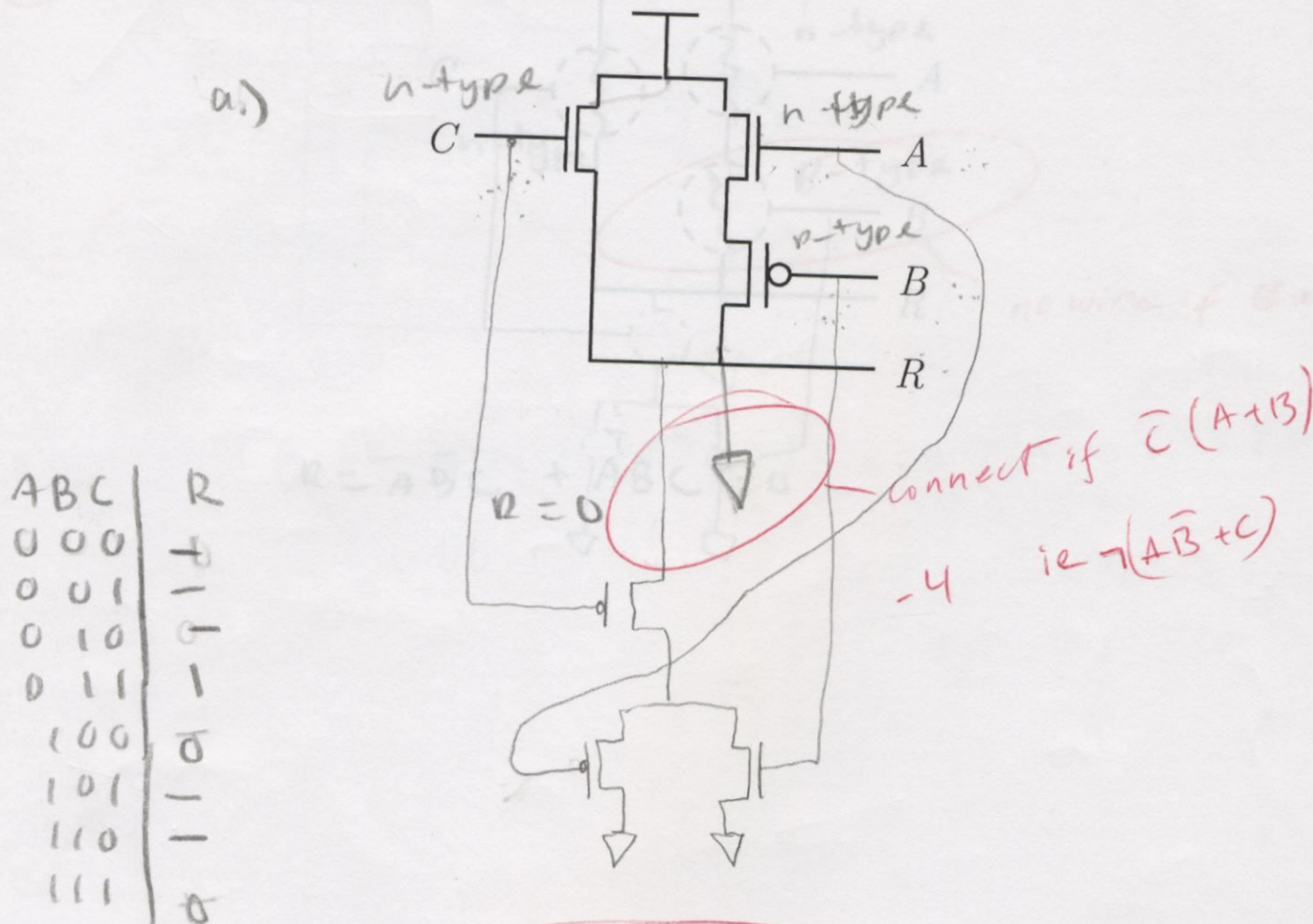9. [9 pts] The transistor diagram below specifies when the output R is supposed to have a value of 1, but the diagram is incomplete: (a) Add wires and transistors as necessary to connect R to ground when R is supposed to have a value of 0. (b) Give a boolean expression description of R using inputs A and B .



b.)

$$R = \bar{A}\bar{B}\bar{C} + ABC$$

$$R = A\bar{B} + C$$

-2


R conn. to power iff $C + A\bar{B}$

R conn. to gnd iff $\neg(C + A\bar{B})$

Midterm Exam


iff $\bar{C}(\bar{A}+B)$

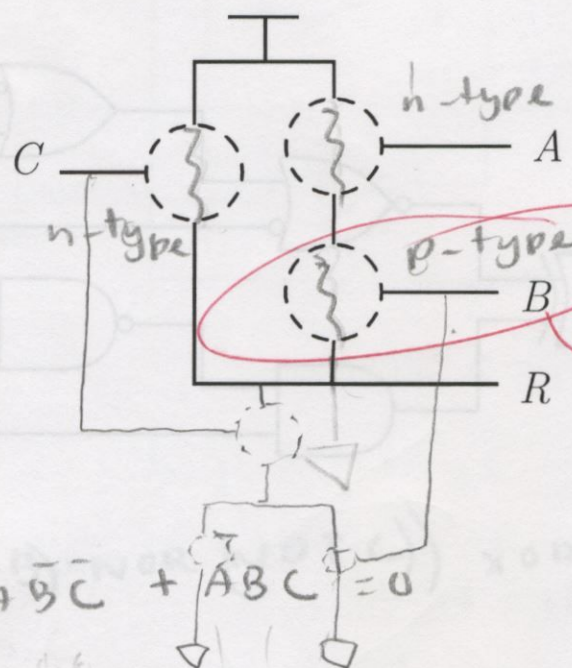10. [8 pts] Complete the wire diagram below so that it describes your circuit from the previous problem ~~when~~ when $A = B = C = 1$.




$$R = \overline{A} \overline{B} \overline{C} + \overline{A} B C = 0$$

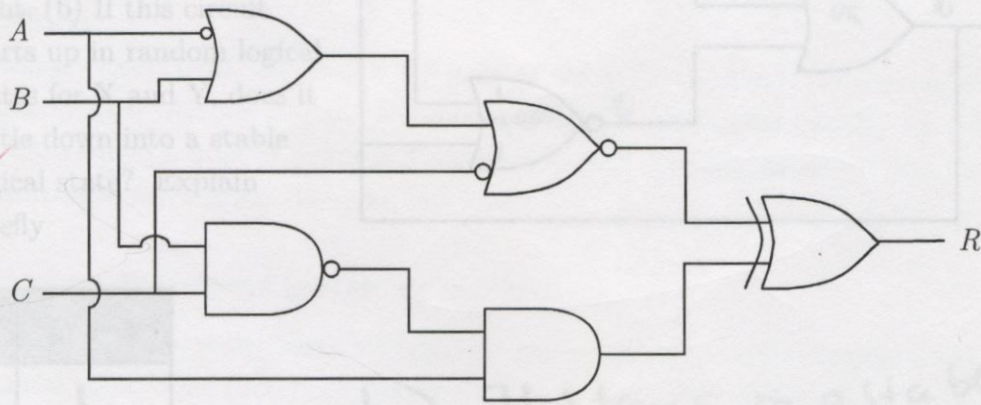11. [6 pts] Translate the logic gate circuit below to a boolean expression for the output R using the inputs A , B , and C .



$$R = ((\text{NOT } A \text{ OR } B) \text{ NOR } (\text{NOT } C)) \text{ XOR } ((B \text{ NAND } C) \text{ AND } A)$$

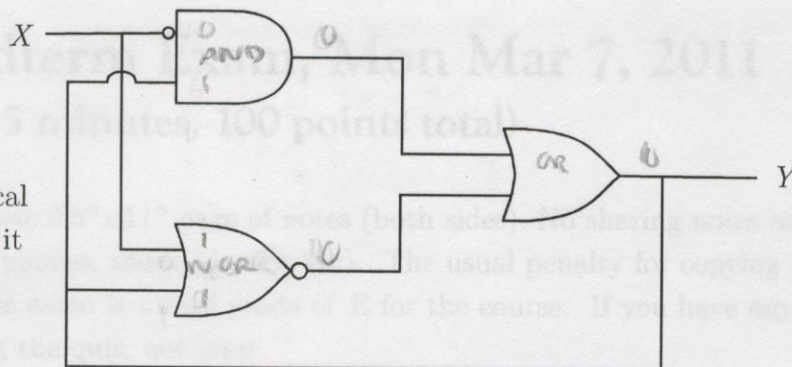12. [7 pts] (a) Fill in the truth table below for the circuit to the right. (b) If this circuit starts up in random logical states for X and Y, does it settle down into a stable logical state? Explain briefly



a.)

X	Y	new Y
0	0	1
0	1	1
1	0	0
1	1	0

b.) It stays in a stable logical state if $x \neq y$ are both 0, or if $x=0$ and $y=1$, $x=1$ and $y=0$, and both $x \neq y$ are 1.

2. [8 pts] Let octal 111 represent a 7-bit 2's complement number. (a) What is the decimal value of this number? (b) Translate this number into 8-bit 2's complement hexadecimal. What is the result?